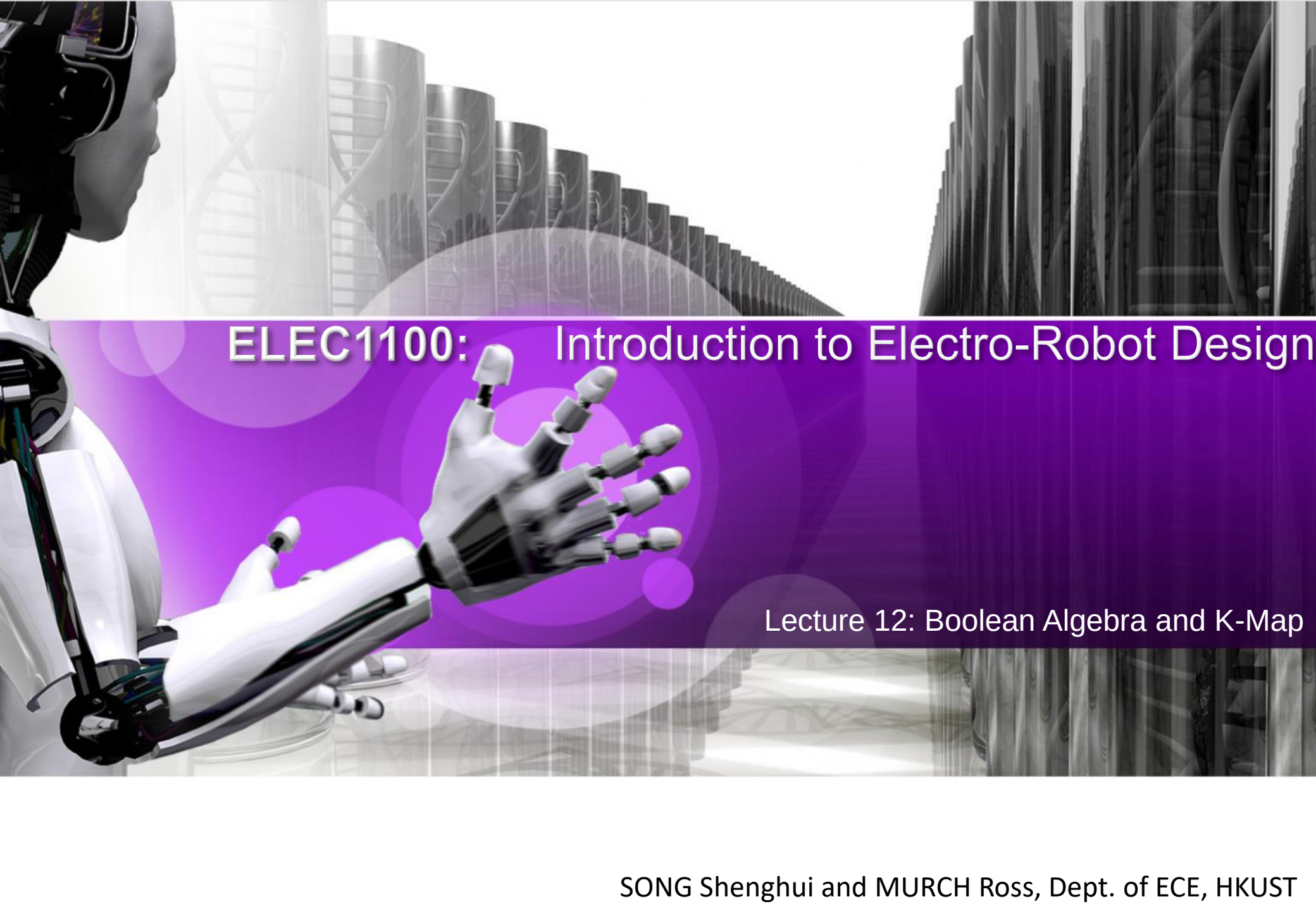





ELEC1100: Introduction to Electro-Robot Design

Lecture 12: Boolean Algebra and K-Map



ELEC1100 ROADMAP

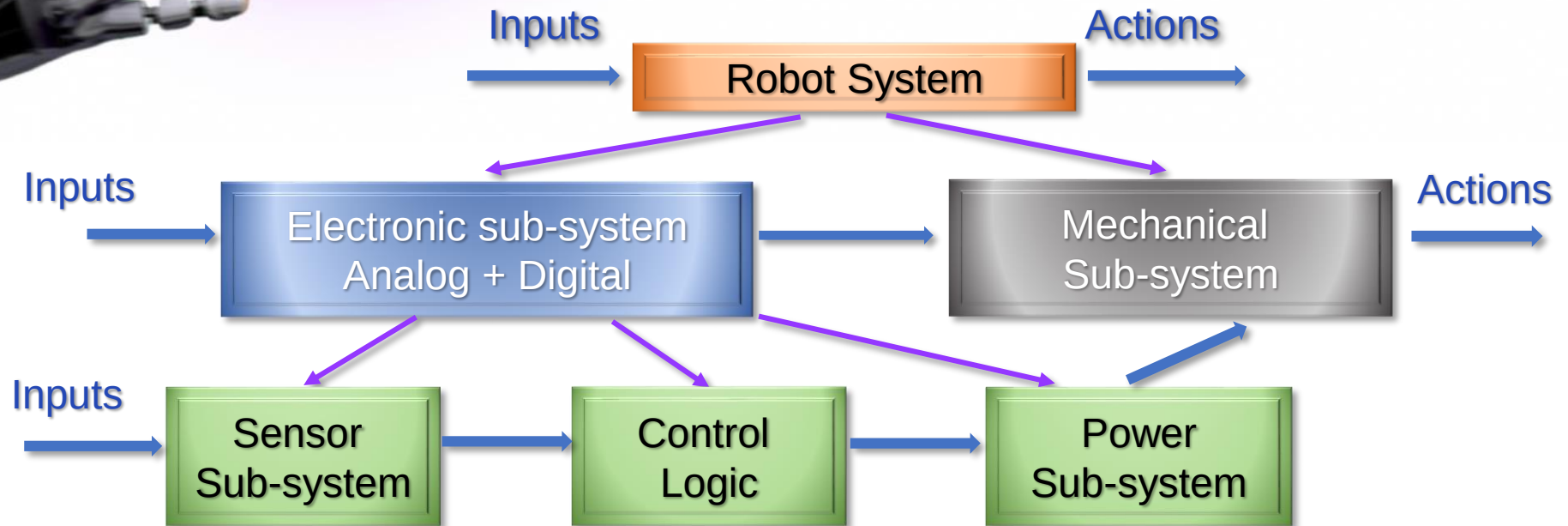

Sensor Basics:

Wk5: Sensor Basic –
Sensor/Line/ADC

Combinational/Sequential Logic:

Wk6: Robot Brain: Logic Gate and
Logic Operation

Basic electronics:

Wk1: Basic Electronics -
Charge/Current/Voltage/Resistor
Wk2: Energy/Power and DC Sources

Motor Power Supply:

Wk3: Pulse Signal and PWM Control
Wk4: Transistor and H-Bridge











FROM LAST LECTURE

❖ Binary digit: 0 and 1 can be represented by logic (True or False)

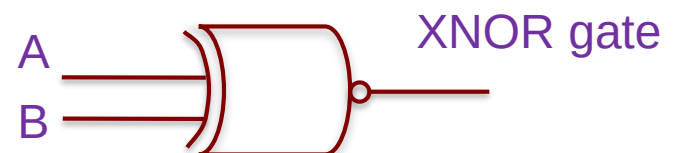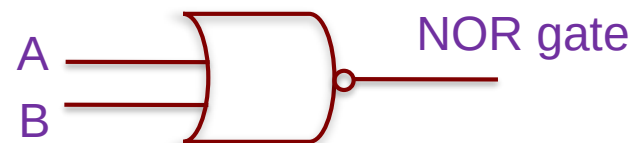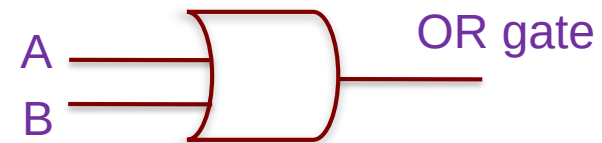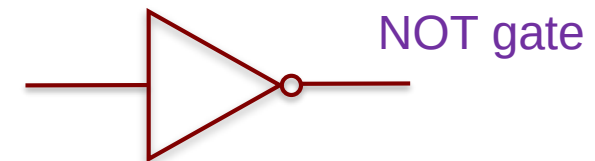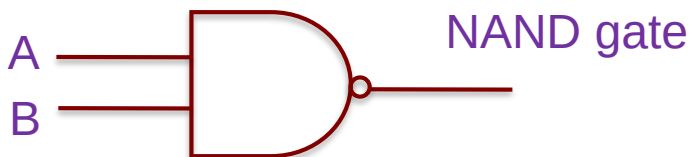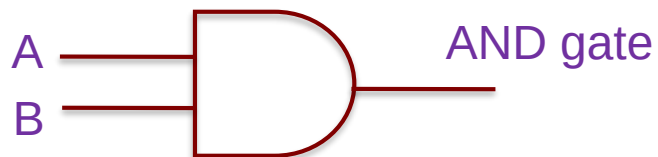
- 0 is equivalent to False
- 1 is equivalent to True





SOME HISTORY [1]

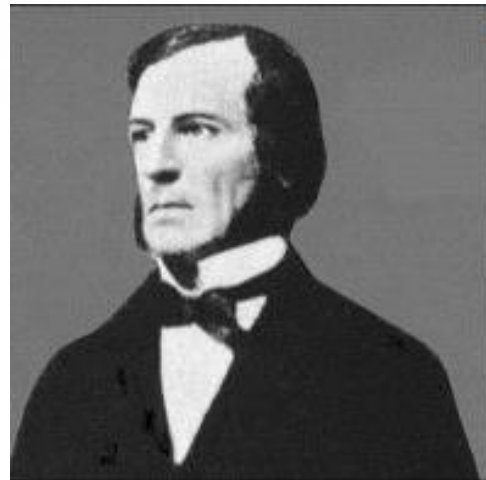- ❖ Boolean algebra was invented by George Boole (1815-1864).
- ❖ Boolean Logic is the basis of modern digital computer logic. Boole is regarded as one of the founders of the field of computer science.





SOME HISTORY [2]


- ❖ Claude Shannon notices similarities between Boolean algebra and electronic telephone switches.
- ❖ Shannon's 1937 MIT Master's Thesis introduces the world to binary digital electronics.
- ❖ It took 30 years to combine Boolean algebra with electronics.
- ❖ IBM's first commercially available scientific computer, 1953 (16,000 adds/sec)





SOME HISTORY [3]

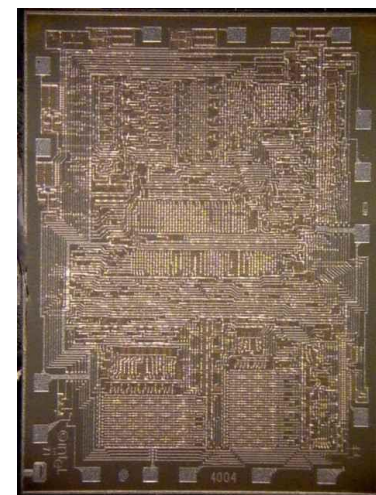
- ❖ First really pocketable calculator
 - Bowmar 901B, 1971
 - Four functions, 8-digit LEDS
 - Costs 3 weeks average wage in America
- ❖ First Microprocessor: Intel 4004, 1971
 - 1K RAM chip and the 4004, a 4-bit microprocessor
 - Clock frequency 740 kHz
 - Two years later comes the 8008, an 8-bit microprocessor
- ❖ Pentium 4 @ 3GHz, 2005: 12×10^9 adds/sec






COMBINATIONAL CIRCUIT

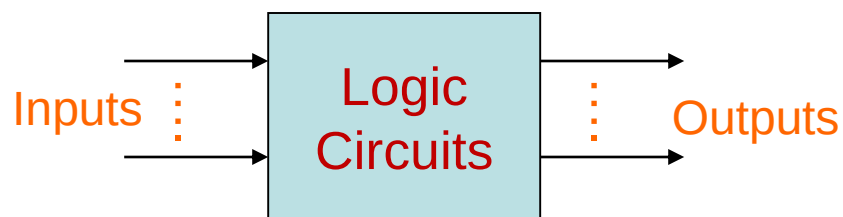- ❖ The outputs depend only on the current inputs of the circuits
- ❖ Output values are expressed by the truth table of the inputs



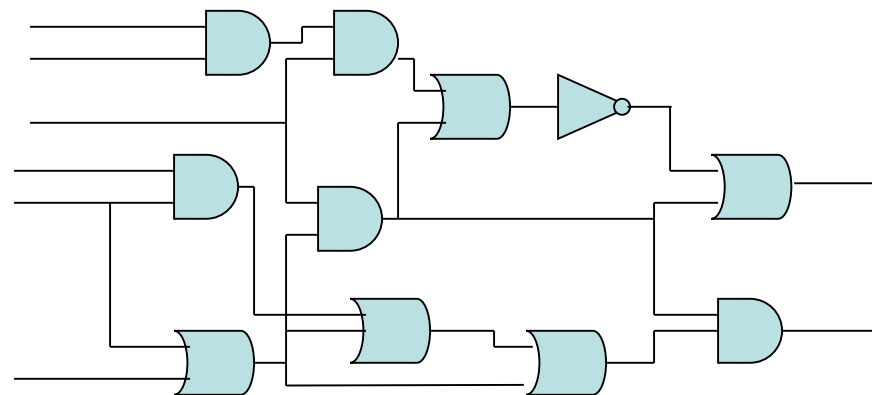- ❖ Logic level of combinational circuit: maximum number of gates of all paths from inputs to outputs of the circuit





Logic level = 5





HOW IS IT RELATED TO YOUR ROBOT?

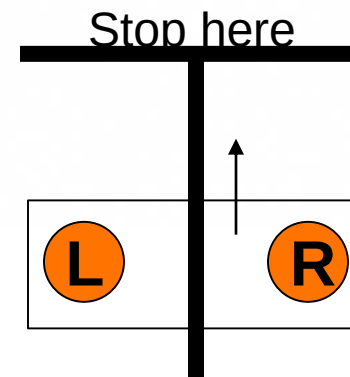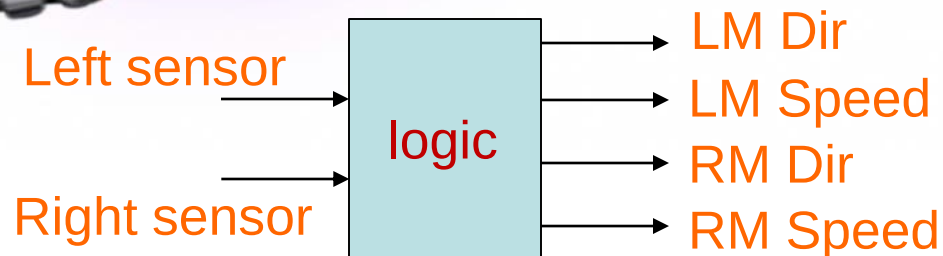

Sensor signal		Actions		Left motor output (L293)		Right motor output (L293)	
Left	Right	Left	Right	Dir	Speed	Dir	Speed
0	0	forward	forward	1	1	1	1
0	1	forward	reverse	1	1	0	1
1	0	reverse	forward	0	1	1	1
1	1	stop	stop	x	0	x	0

(1-detect the line)

(1-Dir forward)

(1-full speed)





COMBINATIONAL LOGIC: STANDARD FORM

- ❖ All Boolean equations can be written in standard forms
- ❖ Sum of Products (SOP) – OR'ing (sum) many AND (product) terms

e.g. $X = A \cdot B + B \cdot C \cdot D + \bar{E} \cdot \bar{F}$

- ❖ Product of Sums (POS) – AND'ing (product) many OR (sum) terms

e.g. $\bar{X} = (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C} + \bar{D}) \cdot (E + F)$

- ❖ How do you change from one form to another?





COMBINATIONAL LOGIC AND TRUTH TABLE

[1]


- ❖ Build the truth table of the following circuit

$$F = (A+B)(C \cdot D)(\bar{A}) + (A \cdot \bar{B})(\bar{A}+B+\bar{D})(A \cdot \bar{C})$$

- ❖ Before you build the truth table, can you simplify F ?

$$F = (A+B)(C \cdot D)(\bar{A}) + (A \cdot \bar{B})(\bar{A}+B+\bar{D})(A \cdot \bar{C})$$
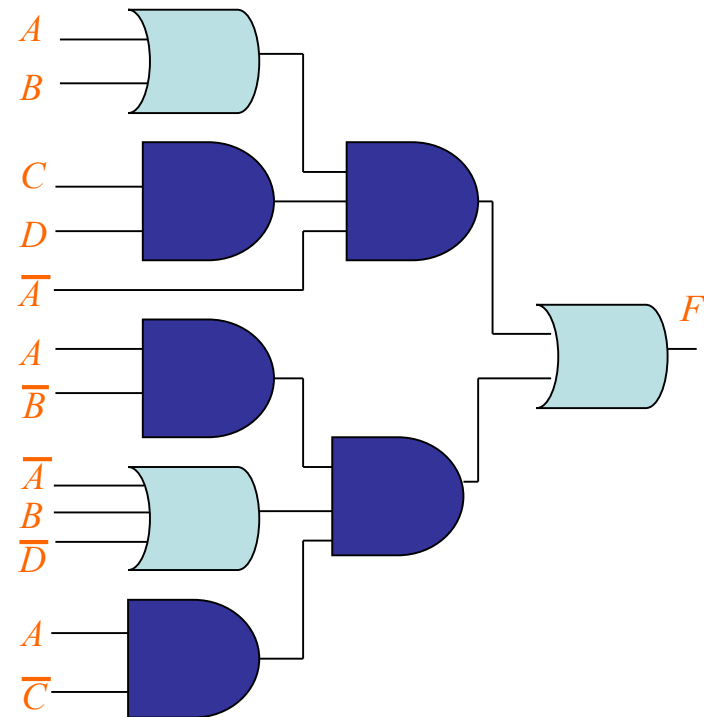
$$= \bar{A}BCD + A\bar{B}\bar{C}\bar{D}$$





COMBINATIONAL LOGIC AND TRUTH TABLE

[2]

$$\begin{aligned} F &= (A+B)(C \cdot D)(\bar{A}) + \\ &\quad (A \cdot \bar{B})(\bar{A}+B+\bar{D})(A \cdot \bar{C}) \\ &= \bar{A}BCD + A\bar{B}\bar{C}\bar{D} \end{aligned}$$

A	B	C	D	$\bar{A}BCD + A\bar{B}\bar{C}\bar{D}$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0





BUILDING CIRCUIT FROM TRUTH TABLE

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- ❖ We can implement using SOP from each '1' at the output term
- ❖ Add it up together means OR'ing all these terms together

$$F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

- ❖ We need 5 **AND** gates, 3 **NOT** gates and 1 **OR** gate,
- ❖ Can we use fewer gates?
- ❖ Is there any systematic way to build a circuit from a truth table?





KARNAUGH MAP (K-MAP)

- ❖ **K-map** can help to convert any Boolean function or truth table into an equivalent SOP form with fewest possible product terms
- ❖ Two-variable K-map

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

	$\overline{A}$	A
$\overline{B}$	1	1
B	1	0



K-map

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

	$\overline{A}$	A
$\overline{B}$	1	0
B	0	0





LOGIC MINIMIZATION USING K-MAP

- ❖ Begin with isolated cells that no simplification is possible.
- ❖ Find all cells that are adjacent to only one other cell, forming two-cell subcubes
- ❖ Find cells that form four-cell subcubes, eight-cell subcubes, etc.
- ❖ Collect the smallest number of maximal subcubes

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1



	$\overline{A}$	A
$\overline{B}$	0	1
B	0	1

$$F = A\overline{B} + AB$$


$$F = A$$

Can you do this?




	$\overline{A}$	A
$\overline{B}$	0	1
B	1	0



K-MAP WITH 3 VARIABLES

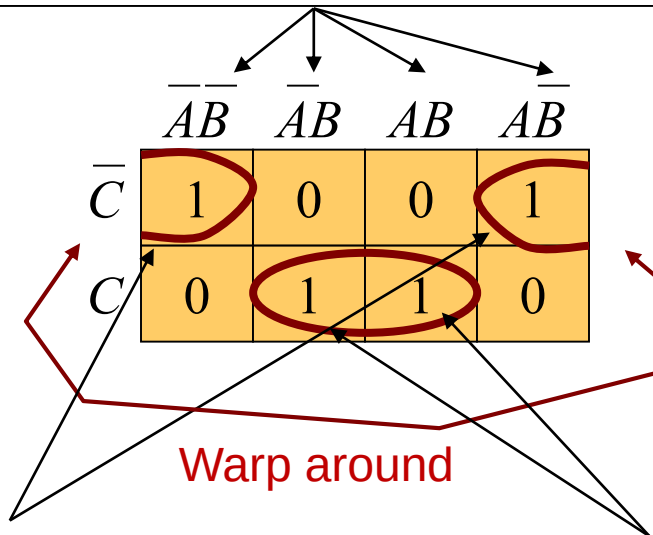Adjacent label should have one and only one variable difference



Before circling:

$$F = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C}$$



After circling:

$$F = \overline{B}\overline{C}$$

Before circling:

$$F = \overline{A}BC + ABC$$



After circling:

$$F = BC$$

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Before circling:

$$F = \overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$



After circling:

$$F = \overline{B}\overline{C} + BC$$






K-MAP WITH 4 VARIABLES

Adjacent label should have one and only one variable difference

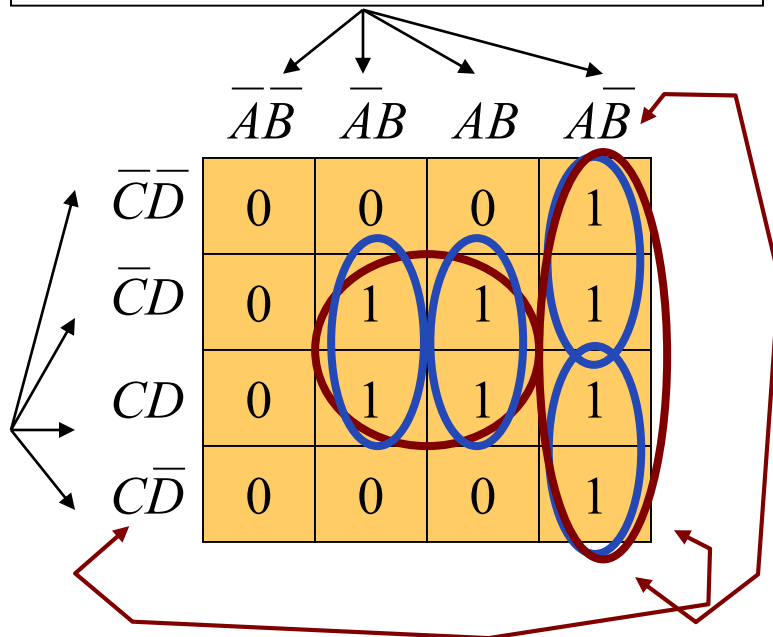Adjacent label should have one and only one variable difference



These cells are adjacent

These cells are adjacent

Before circling:

$$F = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}CD + A\overline{B}\overline{C}D + A\overline{B}CD$$



First circling:

$$F = \overline{A}BD + ABD + A\overline{B}\overline{C} + A\overline{B}C$$



Second circling:

$$F = BD + A\overline{B}$$

Reduce from eight 4-input-AND gates and one 8-input-OR gate to two 2-input-AND gate and one 2-input-OR gate





DON'T CARE (IT IS A WILD CARD)

- ❖ Some combination of inputs maybe impossible for a given situation
- ❖ For example: *A* – door locked, *B* – door open, *F* – you come in
- ❖ Truth Table:

<i>A</i>	<i>B</i>	<i>F</i>
0	0	x
0	1	1
1	0	0
1	1	x

- ❖ It is impossible for a door to be locked and open together, and we “don’t care” about the output in this case
- ❖ You may assign it to either “**0**” or “**1**” to simplify the case





EXAMPLE IN USING DON'T CARE

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	x	1	0	0
$\bar{C}D$	1	1	1	0
CD	0	1	0	0
$C\bar{D}$	0	0	x	0

1 assignment
of don't care

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	0	1	0	0
$\bar{C}D$	1	1	1	0
CD	0	1	0	0
$C\bar{D}$	0	0	1	0

$$F = \bar{A}B\bar{C} + \bar{A}BD + \bar{A}\bar{C}D + B\bar{C}D + ABC\bar{D}$$

another assignment
of don't care

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	1	1	0	0
$\bar{C}D$	1	1	1	0
CD	0	1	0	0
$C\bar{D}$	0	0	0	0

$$F = \bar{A}\bar{C} + B\bar{C}D + \bar{A}BD$$

- ❖ By assigning different values to don't cares, you can simplify the function and the circuit implementation



LECTURE SUMMARY

❖ Logic minimization using K-map

- Begin with isolated cells
- These must be used as they are and no simplification is possible
- Find all cells that are adjacent to only one other cell, forming two-cell subcubes
- Find cells that form four-cell subcubes, eight-cell subcubes, etc.
- Collect the smallest number of maximal subcubes

	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
$\overline{C}\overline{D}$	0	0	0	0
$\overline{C}D$	0	1	1	0
CD	0	1	1	0
$C\overline{D}$	0	0	0	0



NEXT LECTURE

- ❖ Combinational logic
- ❖ Sequential Logic with memory unit
- ❖ MCU and Arduino



QUESTIONS?

